

EE5811 : FPGA LAB

ASSIGNMENT 1

Himanshu Yadav
IS21MTECH11003

January 14, 2022

Problem

Question 6) b) from papers/cbse/cs/2017.pdf

Draw the logic circuit of the following boolean expression using only NOR Gates :


$$(A + B) \cdot (C + D)$$

Solution

To convert the above expression to NOR only logic circuit we will take the Double conjugate of the whole expression and then use de Morgan's Theorem to simplify it.

$$\begin{aligned} & (A + B) \cdot (C + D) \\ & \overline{\overline{(A + B) \cdot (C + D)}} \\ & \overline{\overline{(A + B)} + \overline{\overline{(C + D)}}} \end{aligned}$$

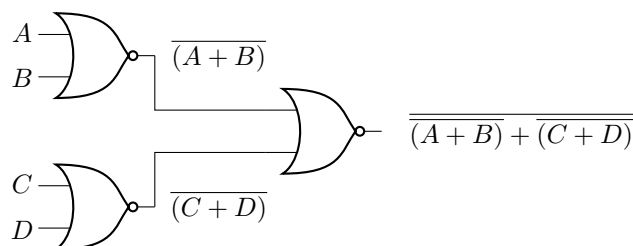The last expression can easily be drawn using NOR gates in the following manner



A C Code has been attached in the repository for verification

`./nor_representation.c`