

EE5811 : FPGA LAB

CHALLENGE PROBLEM 2

Himanshu Yadav
IS21MTECH11003

January 19, 2022


Problem

Is it possible to implement the NAND logic using some data structure/algorithm?

Solution

To answer the above question I have used Struct datatype in C. I have created a NAND Structure with two input elements and a function pointer to calculate the result when required. The code for the same can be seen in NAND_Struct.c file.

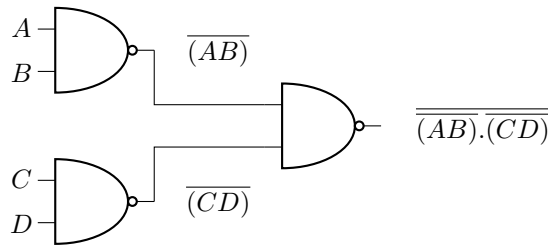One examples have been worked out with : $AB + CD \Leftrightarrow \overline{\overline{AB} \cdot \overline{CD}}$



A	B	C	D	OUT
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Table 1: Truth table for above shown logic

NOTE : C programs are executed sequentially. This should be kept in mind while making gate connections in the code.